

Design Practices for Low-Power External Oscillators

*Author: Jonathan Dillon
Microchip Technology Inc.*

INTRODUCTION

Many Microchip microcontrollers have internal circuitry to drive a 32.768 kHz external crystal to provide an asynchronous clock signal to the Timer1 internal counter. Timer1 is a 16-bit counter which can be used to create a Real-Time Clock (RTC) with a precise, 1-second overflow interrupt for system timing.


OUTLINE

Extremely low-power oscillator circuits, by their nature, do not have high-power drive capability; and as a result, they require attention to detail of low-power design practices and techniques to ensure robust operation. A poorly designed oscillator circuit will have reduced frequency accuracy and may not function correctly over temperature and voltage ranges.

Key features for robust operation are:

1. Dry and moisture-free circuit boards
2. Clean circuit boards that are free of contaminants
3. A quality low-power crystal
4. Load capacitors matched to the crystal and circuit board
5. The crystal supplier's characterization report

FIGURE 1: EXTERNAL CRYSTAL OSCILLATOR CIRCUIT

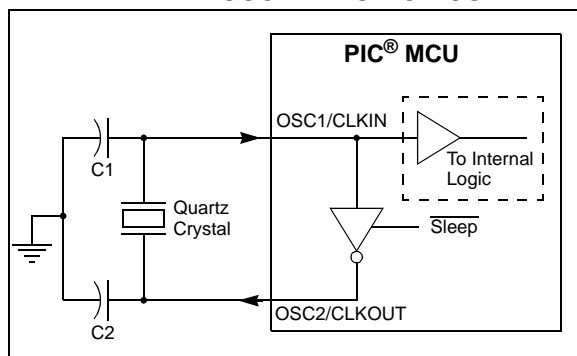

PROBING THE CIRCUIT

Oscillator circuits are highly sensitive to capacitance; therefore, special care needs to be taken when examining signals. A regular oscilloscope probe has 10-12 pF of capacitance, which can be sufficient to stop oscillations. It is recommended that low-capacitance probes be used, preferably with a JFET input, and that the OSC2 pin be probed instead of OSC1.

Many new devices incorporate Automatic Gain Control (AGC) for the crystal oscillator drive circuit; where, to conserve power, the amplitude of the signal is reduced when the circuit is operating as intended. When examining the waveforms, this needs to be considered, as the AGC may be attempting to compensate for an imperfect circuit by increasing the peak to peak drive signal. When adding additional load to the circuit, such as an oscillator probe, the amplitude of the signal will initially be reduced. The AGC will then compensate and increase the amplitude back to its earlier level. This response occurs slow enough to be visible on an oscilloscope.

Dry and Moisture-Free Circuit Boards

Damp circuit boards or moisture condensing onto them at low temperatures can establish leakage paths to ground, which, given the low power of the oscillator drive circuit, can load the circuit greater than the drive strength of the circuit can overcome.

If the circuit boards have been washed, it is then recommended they be allowed to dry thoroughly before being assembled into the system. For low-temperature operation, where moisture condensing may be an issue, conformal coating is recommended (see **Section "Conformal Coating"**).


Clean Circuit Boards that Are Free of Contaminants

Solder flux may leave a residue on the board, which may not easily wash off. Flux remover and scrubbing the board may be required to remove this residue and should remove other contaminants. Some flux residues are weakly conductive; and in the presence of moisture can become highly conductive creating leakage paths.

Load Capacitors Matched to the Crystal and Circuit Board

The crystal needs to see a specific capacitance on either side for maximum frequency accuracy and reliable operation. This should be specified by the crystal manufacturer in the crystal data sheet. Common capacitances are 12.5 pF, 9 pF and 7 pF. Figure 2 shows the affect of capacitance for a 12.5 pF crystal on frequency tolerance.


FIGURE 2: MATCHING OF CAPACITANCE TO CRYSTAL PARAMETERS

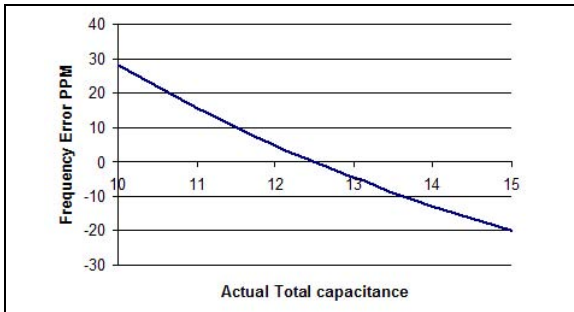

For details on the purpose of these capacitors, please see application note AN943, "Practical PICmicro® Oscillator Analysis and Design."

The capacitor values are very small; and as a result, their value is affected by the capacitance of the bond pads on the microprocessors silicon die and the capacitance of the traces and pads on the circuit board (see Figure 3).

FIGURE 3: REAL OSCILLATOR CIRCUIT DIAGRAM

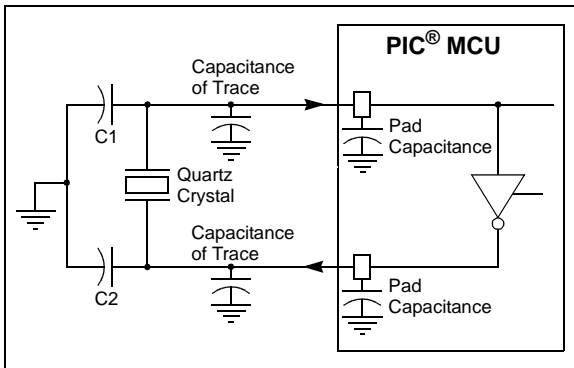

If the traces to the oscillator are kept short, under 10 mm-long each, their capacitance will be very low and almost negligible.

EQUATION 1:

$$\text{Crystal capacitance} = (\text{pad capacitance})/2 + \text{board capacitance} + (C1 * C2)/(C1 + C2)$$

For example, for 8 mm-long traces, the capacitance was measured as 0.85 pF (this is dependant on board layout, material dielectric and thickness). In many cases, the board capacitance can be negligible when the traces are short and surface mount devices are used.

The pad capacitance varies from device to device; but as an example for the PIC18F14K50, the pad capacitance is approximately 2.5 pF per pad.

For example, if a low-power 9 pF crystal in a surface mount package (MS3V-T1R 32.768 kHz 9 pF) is used, then the capacitor values are calculated as follows:

EQUATION 2:

$$9 = 2.5/2 + 0.85 + (C1 * C2)/(C1 + C2)$$

As we are using equal value loading capacitors the math can be simplified to:

EQUATION 3:

$$9 = 1.25 + 0.85 + (C1)/2 \text{ and } C1 = C2$$

Solving:

EQUATION 4:


$$C1 = C2 = 13.6 \text{ pF}$$

Selecting the lowest available standard capacitor value, because of trace capacitance, should give us near the ideal total capacitance seen by the crystal.

A Quality Low-Power Crystal (of the Correct Capacitance) is Used

Low-power external oscillator circuits typically use a 32.768 kHz tuning fork crystal. These crystals are highly accurate. However, their frequency tolerance does vary with temperature, as seen in Figure 4.

FIGURE 4: FREQUENCY TOLERANCE VS. TEMPERATURE

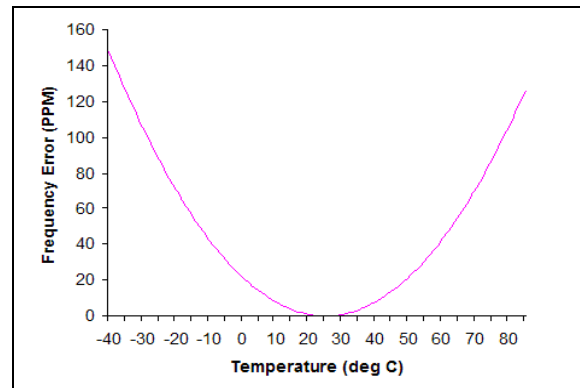

The crystal load capacitance needs to be matched for maximum accuracy, as discussed in **Section “Load Capacitors Matched to the Crystal and Circuit Board”**. For many low-power designs, lower capacitance crystals, 7 pF and 9 pF, are recommended. Low-power crystals with low ESR of less than 65 KOhm are recommended, as they allow for higher oscillation allowance which ensures reliable operation over temperature and voltage. For oscillation allowance, please refer to **Section “The Crystal Manufacturer’s Characterization Report”**.

The Crystal Manufacturer’s Characterization Report

Many crystal manufacturers can provide characterization testing of a design. For an example test report, refer to TB097, “*Interfacing a Micro Crystal MS1V-T1K 32.768 kHz Tuning Fork Crystal to a PIC16F690/SS.*” The manufacturer will need a populated board with the microcontroller programmed to exercise the crystal. Crystal manufacturers typically have the equipment to measure the board and pad capacitances and determine the ideal capacitor value. Negative resistance testing can be used to determine the oscillation allowance and if there is sufficient margin for reliable operation given manufacturing tolerances of the crystal. The oscillator margin required for confident operation is dependant on the number of units tested. For a single unit, the circuit should operate correctly with 5x the crystal ESR that is added via negative resistance testing. Negative resistance testing can also be performed via the methods detailed in application note AN943, “*Practical PICmicro® Oscillator Analysis and Design.*”

CONFORMAL COATING

Conformal coating can be applied to the board to prevent moisture or other contaminants from making electrical contact with the board. Microchip recommends that the sensitive traces and components for the low-power oscillator circuit be coated to prevent moisture and other contaminants from increasing the loading on the drive circuit by creating leakage paths across the board. This includes the crystal’s pads or leads, the traces on the board, and the back of the board if through hole devices or vias are used. If LP Oscillator mode is used then pins OSC1 and OSC2 should be coated, or pins T1OSCI and T1OSCO if Timer1 uses different pins for an external oscillator.

Conformal coatings can be applied via:

- **Dipping**
 - Gives the best coverage but requires complicated masking

- **Spraying**

- For most prototyping and small volume, spraying is the most common method; although, care needs to be taken to ensure thorough coverage. Both acrylic and silicone-based coatings are available in spray-can form. For large scale production, there are atomizing spray systems which can be programmed to take defined paths across the board and to cover specific areas.

- **Brushing**

- Conformal coatings may be brushed over sensitive areas of the board; however, this is the least reliable method since brush marks may leave small gaps in the coating.

A conformal coating that luminesces under UV light is recommended to aid in quality control inspection. The coverage of vertical surfaces of the device pins and leads can be problematic with less viscous coatings; but can be improved by inverting the board to dry after spraying. Conformal coatings can also provide mechanical support for components. However, connectors and contact points will require masking off so they can be used after coating. Since only high-impedance signals and sensitive circuitry needs to be coated, the rest of the board can be masked off; although, there may be some leakage of the coating. The coating may require removal for board modifications and the method used should be recommended by the coating manufacturer, though it is usually a recommendation for a specific solvent.

The other option for harsh wet environments is to use a potting compound to seal the board. These are typically epoxy-based and removal of the compound is extremely difficult should the board require modifications or rework, and provision needs to be made to access connectors.

The boards need to be clean and dry before coating, otherwise contamination will be sealed in and may cause later problems.

Conformal coatings and potting compounds need to be adequately cured as directed by the manufacturer. Otherwise, they may have inferior electrical performance, especially in high humidity or low-temperature environments.

CONCLUSION

Low-power crystal oscillators offer extended battery life and lower current consumption for applications requiring a Real-Time Clock or to wake the device from Sleep at specific intervals.

Low-power nature crystal oscillators are less tolerant of incorrect crystal types, load capacitors and contaminants on the circuit board.

AN1288

NOTES:

Note the following details of the code protection feature on Microchip devices:

- Microchip products meet the specification contained in their particular Microchip Data Sheet.
- Microchip believes that its family of products is one of the most secure families of its kind on the market today, when used in the intended manner and under normal conditions.
- There are dishonest and possibly illegal methods used to breach the code protection feature. All of these methods, to our knowledge, require using the Microchip products in a manner outside the operating specifications contained in Microchip's Data Sheets. Most likely, the person doing so is engaged in theft of intellectual property.
- Microchip is willing to work with the customer who is concerned about the integrity of their code.
- Neither Microchip nor any other semiconductor manufacturer can guarantee the security of their code. Code protection does not mean that we are guaranteeing the product as "unbreakable."

Code protection is constantly evolving. We at Microchip are committed to continuously improving the code protection features of our products. Attempts to break Microchip's code protection feature may be a violation of the Digital Millennium Copyright Act. If such acts allow unauthorized access to your software or other copyrighted work, you may have a right to sue for relief under that Act.

Information contained in this publication regarding device applications and the like is provided only for your convenience and may be superseded by updates. It is your responsibility to ensure that your application meets with your specifications. MICROCHIP MAKES NO REPRESENTATIONS OR WARRANTIES OF ANY KIND WHETHER EXPRESS OR IMPLIED, WRITTEN OR ORAL, STATUTORY OR OTHERWISE, RELATED TO THE INFORMATION, INCLUDING BUT NOT LIMITED TO ITS CONDITION, QUALITY, PERFORMANCE, MERCHANTABILITY OR FITNESS FOR PURPOSE. Microchip disclaims all liability arising from this information and its use. Use of Microchip devices in life support and/or safety applications is entirely at the buyer's risk, and the buyer agrees to defend, indemnify and hold harmless Microchip from any and all damages, claims, suits, or expenses resulting from such use. No licenses are conveyed, implicitly or otherwise, under any Microchip intellectual property rights.

Trademarks

The Microchip name and logo, the Microchip logo, dsPIC, KEELOQ, KEELOQ logo, MPLAB, PIC, PICmicro, PICSTART, rfPIC and UNI/O are registered trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.


FilterLab, Hampshire, HI-TECH C, Linear Active Thermistor, MXDEV, MXLAB, SEEVAL and The Embedded Control Solutions Company are registered trademarks of Microchip Technology Incorporated in the U.S.A.

Analog-for-the-Digital Age, Application Maestro, CodeGuard, dsPICDEM, dsPICDEM.net, dsPICworks, dsSPEAK, ECAN, ECONOMONITOR, FanSense, HI-TIDE, In-Circuit Serial Programming, ICSP, Mindi, MiWi, MPASM, MPLAB Certified logo, MPLIB, MPLINK, mTouch, Octopus, Omniscient Code Generation, PICC, PICC-18, PICDEM, PICDEM.net, PICkit, PICtail, PIC³² logo, REAL ICE, rLAB, Select Mode, Total Endurance, TSHARC, UniWinDriver, WiperLock and ZENA are trademarks of Microchip Technology Incorporated in the U.S.A. and other countries.

SQTP is a service mark of Microchip Technology Incorporated in the U.S.A.

All other trademarks mentioned herein are property of their respective companies.

© 2009, Microchip Technology Incorporated, Printed in the U.S.A., All Rights Reserved.

 Printed on recycled paper.

QUALITY MANAGEMENT SYSTEM
CERTIFIED BY DNV
== ISO/TS 16949:2002 ==

Microchip received ISO/TS-16949:2002 certification for its worldwide headquarters, design and wafer fabrication facilities in Chandler and Tempe, Arizona; Gresham, Oregon and design centers in California and India. The Company's quality system processes and procedures are for its PIC® MCUs and dsPIC® DSCs, KEELOQ® code hopping devices, Serial EEPROMs, microperipherals, nonvolatile memory and analog products. In addition, Microchip's quality system for the design and manufacture of development systems is ISO 9001:2000 certified.



WORLDWIDE SALES AND SERVICE

AMERICAS

Corporate Office

2355 West Chandler Blvd.
Chandler, AZ 85224-6199
Tel: 480-792-7200
Fax: 480-792-7277
Technical Support:
<http://support.microchip.com>
Web Address:
www.microchip.com

Atlanta

Duluth, GA
Tel: 678-957-9614
Fax: 678-957-1455

Boston

Westborough, MA
Tel: 774-760-0087
Fax: 774-760-0088

Chicago

Itasca, IL
Tel: 630-285-0071
Fax: 630-285-0075

Cleveland

Independence, OH
Tel: 216-447-0464
Fax: 216-447-0643

Dallas

Addison, TX
Tel: 972-818-7423
Fax: 972-818-2924

Detroit

Farmington Hills, MI
Tel: 248-538-2250
Fax: 248-538-2260

Kokomo

Kokomo, IN
Tel: 765-864-8360
Fax: 765-864-8387

Los Angeles

Mission Viejo, CA
Tel: 949-462-9523
Fax: 949-462-9608

Santa Clara

Santa Clara, CA
Tel: 408-961-6444
Fax: 408-961-6445

Toronto

Mississauga, Ontario,
Canada
Tel: 905-673-0699
Fax: 905-673-6509

ASIA/PACIFIC

Asia Pacific Office

Suites 3707-14, 37th Floor
Tower 6, The Gateway
Harbour City, Kowloon
Hong Kong
Tel: 852-2401-1200
Fax: 852-2401-3431

Australia - Sydney

Tel: 61-2-9868-6733
Fax: 61-2-9868-6755

China - Beijing

Tel: 86-10-8528-2100
Fax: 86-10-8528-2104

China - Chengdu

Tel: 86-28-8665-5511
Fax: 86-28-8665-7889

China - Hong Kong SAR

Tel: 852-2401-1200
Fax: 852-2401-3431

China - Nanjing

Tel: 86-25-8473-2460
Fax: 86-25-8473-2470

China - Qingdao

Tel: 86-532-8502-7355
Fax: 86-532-8502-7205

China - Shanghai

Tel: 86-21-5407-5533
Fax: 86-21-5407-5066

China - Shenyang

Tel: 86-24-2334-2829
Fax: 86-24-2334-2393

China - Shenzhen

Tel: 86-755-8203-2660
Fax: 86-755-8203-1760

China - Wuhan

Tel: 86-27-5980-5300
Fax: 86-27-5980-5118

China - Xiamen

Tel: 86-592-2388138
Fax: 86-592-2388130

China - Xian

Tel: 86-29-8833-7252
Fax: 86-29-8833-7256

China - Zhuhai

Tel: 86-756-3210040
Fax: 86-756-3210049

ASIA/PACIFIC

India - Bangalore

Tel: 91-80-3090-4444
Fax: 91-80-3090-4080

India - New Delhi

Tel: 91-11-4160-8631
Fax: 91-11-4160-8632

India - Pune

Tel: 91-20-2566-1512
Fax: 91-20-2566-1513

Japan - Yokohama

Tel: 81-45-471- 6166
Fax: 81-45-471-6122

Korea - Daegu

Tel: 82-53-744-4301
Fax: 82-53-744-4302

Korea - Seoul

Tel: 82-2-554-7200
Fax: 82-2-558-5932 or
82-2-558-5934

Malaysia - Kuala Lumpur

Tel: 60-3-6201-9857
Fax: 60-3-6201-9859

Malaysia - Penang

Tel: 60-4-227-8870
Fax: 60-4-227-4068

Philippines - Manila

Tel: 63-2-634-9065
Fax: 63-2-634-9069

Singapore

Tel: 65-6334-8870
Fax: 65-6334-8850

Taiwan - Hsin Chu

Tel: 886-3-6578-300
Fax: 886-3-6578-370

Taiwan - Kaohsiung

Tel: 886-7-536-4818
Fax: 886-7-536-4803

Taiwan - Taipei

Tel: 886-2-2500-6610
Fax: 886-2-2508-0102

Thailand - Bangkok

Tel: 66-2-694-1351
Fax: 66-2-694-1350

EUROPE

Austria - Wels

Tel: 43-7242-2244-39
Fax: 43-7242-2244-393

Denmark - Copenhagen

Tel: 45-4450-2828
Fax: 45-4485-2829

France - Paris

Tel: 33-1-69-53-63-20
Fax: 33-1-69-30-90-79

Germany - Munich

Tel: 49-89-627-144-0
Fax: 49-89-627-144-44

Italy - Milan

Tel: 39-0331-742611
Fax: 39-0331-466781

Netherlands - Drunen

Tel: 31-416-690399
Fax: 31-416-690340

Spain - Madrid

Tel: 34-91-708-08-90
Fax: 34-91-708-08-91

UK - Wokingham

Tel: 44-118-921-5869
Fax: 44-118-921-5820

03/26/09